

## Lab 7 Report

### Problem Summary and System Specifications:

For this lab, I built upon my arithmetic logic unit (ALU) by implementing a “first-in, first-out” (FIFO) memory unit and a reset module. The ALU is expected to add and subtract 6-bit values the same way it did in lab 4. For the purposes of lab 7, I have added four logical operation modules into my design. The FIFO, which incorporates similar modules from lab 6, allows me to store operations into memory and execute these operations all at once. The reset function allows me to clear all operations from my system memory.

The following is a list of system design specifications:

1. Inputs:
  - a. 2 6-bit two's complement numbers
  - b. 1 3-bit operations number
    - i. Add = 000
    - ii. Subtract = 001
    - iii. Equal = 100
    - iv. Greater than = 101
    - v. Less than = 110
    - vi. A equal 0 = 111
  - c. 1 mode switch to determine read or write state
  - d. 1 push-button to read from or write to memory
  - e. 1 reset switch
2. Outputs:
  - a. 6 7-segment displays
    - i. 2 for each of the 6-bit two's complement numbers
    - ii. 2 for the result of the operation
  - b. 6 LEDs
    - i. 1 for indicating negative values for each of the 6-bit two's complement numbers
    - ii. 1 for indicating a negative value for the result of the operation
    - iii. 1 for indicating overflow of the result of the operation
    - iv. 1 for indicating FIFO is full
    - v. 1 for indicating FIFO is empty
3. 2 FSMs:

- a. 1 for determining state of logical operation
- b. 1 for determining read or write state
4. FIFO to store up to 8 operations at one time
5. Reset that uses asynchronous assert and synchronous deassert

### System Design:

Essentially, this lab merges the ALU design of lab 4 with the memory feature of lab 6. In addition to being able to add and subtract, the ALU is capable of a series of comparison operations. These operations will output a “1” to the 7-segment LEDs if the calculation is true and “0” if the calculation is false. The *equal* operation compares the two input values, denoted as A and B, and determines if they are the same values. The *greater than* operation compares A and B and determines whether or not A is greater than B, while the *less than* operation determines if A is less than B. Lastly, the *zero* operation determines if A is equal to 0.

### Lab 7 Block Diagram

Bryan Ching


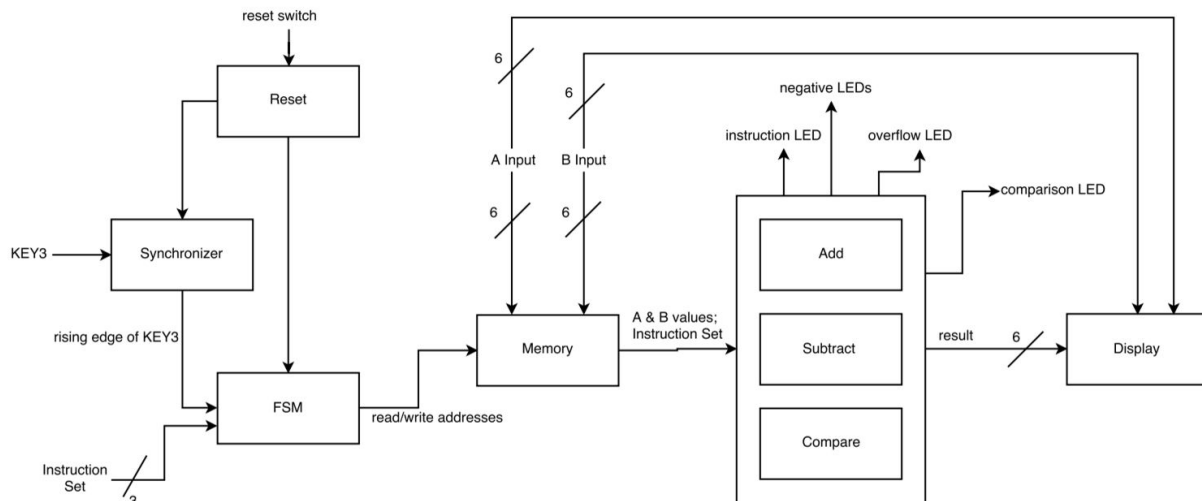


Figure 1: Lab 7 Block Diagram

The block diagram in Figure 1 depicts the initial layout of this lab, which incorporates a memory feature with the ALU. I operate this system by setting the input values, A and B, to whatever 6-bit values I want to calculate. Secondly, I select which 3-bit operation I want to perform. Next, I flip the input switch for writing to memory and press the push-button to perform the operation. If I wish to read the values out of memory and calculate the result, then I flip the switch to read mode and press the push-button again. The corresponding result along with the two input values

display on the 7-segment LEDs. Similar to lab 4, this lab will have LEDs that signify if the values are negative. I added the reset feature at the end of my design in order to revert the entire system back to its initial state, which emptied all values stored in memory.

 

**Figure 2: RTL Viewer**

Figure 2 depicts the RTL viewer for the entire lab 7. There were a couple design changes between the initial conception and the final design. One of these changes is the inclusion of a second Finite State Machine (FSM). Originally, I had one FSM that determined which operation the system will perform. I neglected to include a FSM that determines whether the system is in read or write mode. Secondly, I had to connect my operations FSM differently than how I did in the initial design. Initially, the operations FSM fed into the memory module. I realized that I needed to select either the read or the write mode first, which meant feeding the output of the read/write FSM into the memory module. When I pushed the push-button, the values are read out of memory and feeds into the operations FSM. At this point, the operations FSM performs the proper calculations.

```

1 module fsm_lab7 (input logic clock,
2                 input logic mode, rstsync,
3                 input logic [14:0]dataOut,
4                 output logic [2:0]out_instruct);
5
6     logic [2:0]instruct;
7
8     typedef enum logic [2:0]{Add, Subtract, Equal, Greater, Less, A_0} statetype;
9
10    statetype state, nextstate;
11
12    always_ff @(posedge clock or negedge rstsync)
13    begin
14        if (!rstsync)
15            state <= Add;
16        else
17            state <= nextstate;
18    end
19
20    assign instruct = dataOut[2:0];
21
22    always_comb
23    begin
24        case(state)
25        Add:
26            if (instruct==3'b001 && mode==1'b0)
27                nextstate = Subtract;
28            else if (instruct==3'b100 && mode==1'b0)
29                nextstate = Equal;
30            else if (instruct==3'b101 && mode==1'b0)
31                nextstate = Greater;
32            else if (instruct==3'b110 && mode==1'b0)
33                nextstate = Less;
34            else if (instruct==3'b111 && mode==1'b0)
35                nextstate = A_0;

```

**Figure 3: Operations FSM Code Snippet**

A snippet of code for the operations FSM can be found in Figure 3. The reset module has been implemented into its design. Additionally, each condition statement in the *Add* state as well as the other five states has a *mode* variable. This variable determines whether the system is in read or write mode. “0” denotes the read mode, while “1” denotes the write mode. None of these operations will occur unless the system is reading values from memory. Lastly, this FSM outputs the operation instruction that I input into memory. The top-level module uses this output.

The Read-Write FSM can be found in Appendix A under Figure A-1. I have not edited much in that FSM other than adding the reset functionality. Similarly, the synchronizer code snippet can be found in Appendix A under Figure A-2. The synchronizer does not differ much from my other synchronizer designs from pass labs. The push-button is the only component synchronized with three flip-flops in the whole lab.

```

1 module reset_lab7(input logic clock, rst,
2                  output logic rstsync);
3
4     logic intrRst;
5     always_ff@(posedge clock or negedge rst)
6     if (!rst)
7     begin
8         intrRst <= 1'b0;
9         rstsync <= 1'b0;
10    end
11    else
12    begin
13        intrRst <= 1'b1;
14        rstsync <= intrRst;
15    end
16 endmodule
17
18

```

**Figure 4: Reset Module Code Snippet**

```
1 module memory(input logic clock, ren, wen,  
2               input logic [14:0] dataIn,  
3               input logic [2:0] wrAddr, rdAddr,  
4               output logic [14:0] dataOut);  
5  
6     logic [14:0] memory [7:0];  
7  
8     initial  
9     begin  
10        for (int i=15'b0; i<15'd8; i++)  
11            memory[i] <= i;  
12        end  
13  
14        always_ff @(posedge clock)  
15        begin  
16            if(wen)  
17                memory[wrAddr] <= dataIn;  
18  
19            if(ren)  
20                dataOut <= memory[rdAddr];  
21        end  
22    endmodule  
23  
24
```

**Figure 5: Memory Module Code Snippet**

This reset module is the exact same design as the one used in lab 6 for the memory functionality. This reset uses an asynchronous assert and a synchronous deassert. The asynchronous assert handles the issue of the reset assertion time window. The reset needs to be asserted for multiple clock cycles. The synchronous deassert handles the issue in which the reset deasserts within a recovery time window. The memory module, as depicted in Figure 5, is the only module that uses a flip-flop but does not implement the reset module. This is because Quartus looks for specific code structures to infer as memory. As a result, the reset module cannot be used in the memory module.

```

1 module greater (input logic [5:0]A,
2                 input logic [5:0]B,
3                 output logic [5:0]result,
4                 output logic nA_LED, nB_LED);
5
6     logic [5:0]new_A;
7     logic [5:0]new_B;
8
9     always_comb
10    begin
11        if (A[5] == 1'b1)
12            new_A = ~A+1'b1;
13        else
14            new_A = A;
15    end
16
17    always_comb
18    begin
19        if (B[5] == 1'b1)
20            new_B = ~B+1'b1;
21        else
22            new_B = B;
23    end
24
25    always_comb
26    begin
27        if (A[5] == B[5] && A[5] == 1'b0)
28            begin
29                if (new_A > new_B)
30                    result = 6'd1;
31                else
32                    result = 6'd0;
33            end
34        else if (A[5] == B[5] && A[5] == 1'b1)
35            begin
36                if (new_A > new_B)
37                    result = 6'd1;
38            end
39    end
40
41    nA_LED = result[5];
42    nB_LED = result[5];
43 end

```

**Figure 6: Greater Than Module Code Snippet**

In the *greater than* and *less than* modules, I first calculate the two's complement of both the input values, A and B. My combinational logic involves checking the most significant bit and checking if they are equal to "0" or "1". By doing so, I can confirm whether one or the other is positive or negative. If they are both either positive or negative, then I can do further comparisons. However, if they differ in value, then it is much simpler to determine which input value is greater or less than the other input value. In these two modules, I also determine whether the values are negative and set the negative LED values accordingly. The *less than* module is similar in design with slight difference. As a result, I have placed the screenshot of the *less than* module in Appendix A under Figure A-3.

```

1 module equal (input logic [5:0]A, B,
2               output logic [5:0] result,
3               output logic nA_LED, nB_LED);
4
5     always_comb
6     begin
7         if (A == B)
8             result = 6'd1; // true
9         else
10            result = 6'd0; // false
11    end
12
13    nA_LED = result[5];
14    nB_LED = result[5];
15 end

```

**Figure 7: Equal Module Code Snippet**

```

1 module zero ( input logic [5:0]A,
2               output logic [5:0]result,
3               output logic nA_LED);
4
5 always_comb
6 begin
7     if (A == 6'd0)
8         result = 6'd1;
9     else
10        result = 6'd0;
11 end
12

```

**Figure 8: Zero Module Code Snippet**

The *equal* and *zero* modules are very simple in design. The *equal* module checks if A and B are equal. The *zero* module checks if A is equal to “0”. There are no additional code to determine the two’s complement. These two modules also calculate whether or not their respective negative LEDs need to be turned on, which is later used in the top-level module.

The *adder* and *subtractor* modules are direct copies of the same modules used in lab 4. As such, screenshots of these modules have been included. Their calculations are inherently simple. The *adder* adds the two input values. The *subtractor* needs to take the two’s complement of the second input, B. The module then adds the input, A, and the two’s complement of input B together. Additional calculations in both modules involve calculating whether or not there is overflow and if any of the inputs or output is negative.

```

1 module display ( input logic [5:0]A,
2                 input logic [5:0]B,
3                 input logic [5:0]result,
4                 output logic [6:0]DA7, // A
5                 output logic [6:0]DA6,
6                 output logic [6:0]DA5, // B
7                 output logic [6:0]DA4,
8                 output logic [6:0]DA3, // Result
9                 output logic [6:0]DA2);
10
11 // For Result
12 logic [5:0]new_result;
13 logic [3:0]digit_1; // first digit (tens)
14 logic [3:0]digit_2; // second digit (ones)
15 logic [6:0]display_1; // 7 segment display
16 logic [6:0]display_2;
17

```

**Figure 9: Display Module Code Snippet**



```

1  module decimal (input logic [3:0]digit,
2                  output logic [6:0]display);
3
4      always_comb
5      begin
6          if (digit == 4'd0)
7              display = 7'b1000000; // 0
8          else if (digit == 4'd1)
9              display = 7'b1111001; // 1
10         else if (digit == 4'd2)
11             display = 7'b0100100; // 2
12         else if (digit == 4'd3)
13             display = 7'b0110000; // 3
14         else if (digit == 4'd4)
15             display = 7'b0011001; // 4
16         else if (digit == 4'd5)
17             display = 7'b0010010; // 5
18         else if (digit == 4'd6)
19             display = 7'b0000010; // 6
20         else if (digit == 4'd7)
21             display = 7'b1111000; // 7
22         else if (digit == 4'd8)
23             display = 7'b0000000; // 8
24         else if (digit == 4'd9)
25             display = 7'b0010000; // 9
26         else
27             display = 7'b1111111; // nothing
28     end
29 endmodule
30
31

```

**Figure 10: Decimal Module Code Snippet**

Figure 9 and Figure 10 depict the SystemVerilog code snippets for displaying values on the 7-segment displays. I used six 7-segment displays in my overall design. Each input values and the calculation output value receive two 7-segment displays. The *display* module calculates the tens and the ones digit of the 6-bit inputs and result. Then, it sends those tens and ones digits to the *decimal* module that matches the digits to its corresponding 7-segment combination. The *decimal* module sends the 7-segment combination back to the *display* module to output.

```

118  else
119      begin
120          nA_LED <= nA_LED_Zero;
121          nB_LED <= 1'b0;
122          nR_LED <= 1'b0;
123          over_LED <= 1'b0;
124          DA7 <= display7;
125          DA6 <= display6;
126          DA5 <= display5;
127          DA4 <= display4;
128          DA3 <= display3;
129          DA2 <= display2;
130      end
131  end
132
133  assign LED_full = full;
134  assign LED_empty = empty;
135  assign in_A = dataout[14:9];
136  assign in_B = dataout[8:3];
137
138  fsm_lab7 module1 (.clock(clock), .mode(mode), .rstsync(rstsync), .dataout(dataOut), .out_instruct(out_instr);
139
140  fsm_rw_lab7 module11 (.clock(clock), .mode(mode), .button(rise), .rstsync(rstsync), .ren(ren), .wen(wen),
141                      .empty(empty), .full(full), .r_addr(r_addr), .w_addr(w_addr));
142
143  synchronizer_lab7 module2 (.clock(clock), .button(button), .rstsync(rstsync), .rise(rise));
144
145  memory module3 (.clock(clock), .ren(ren), .wen(wen), .dataIn({A, B, instruct}), .wrAddr(w_addr),
146                 .rdAddr(r_addr), .dataOut(dataOut));
147

```

**Figure 11: Top-Level Module Code Snippet**



Finally, a snippet of code for the top-level module is shown in Figure 11. The top-level combines every one of the aforementioned modules and creates a unified system. Additional calculations that I inputted for the top-level module includes determining the result variable, 7-segment displays, and LEDs based on which operation instruction I select. I determine the result variable value inside an “always\_comb” block, while I determine the LEDs and 7-segment displays inside an “always\_ff” block. Also, this “always\_ff” block implements the reset functionality.

### Testing Approach:

For testing my lab design, I created testbenches for the newer comparison modules, the operations FSM, and the top-level module. The comparison modules that I tested include the *equal*, *greater than*, *less than*, and *zero* modules. For the comparison modules, I designed the testbenches to test basic functionality of each module. I achieved this by testing as many different types of inputs combinations as possible, which includes negative values to ensure the LEDs work as intended as well. With all these different input combinations, I ensure that the modules perform their intended purpose as stated in the system design.

```

module greater_testbench();

    // DUT signals
    logic clock = 1'b0;
    logic [5:0]A;
    logic [5:0]B;
    logic result;

    // Connect device to check
    greater dutlab7(.A(A), .B(B), .result(result));

    // Generate clock
    always #50 clock <= ~clock;

    // Generate inputs

    // Create task to loop through all possible combinations
    task testCase(input logic [5:0]in_A, input logic [5:0]in_B, input logic result_test);
        @(negedge clock);
        A <= in_A;
        B <= in_B;
        @(posedge clock);
        check: assert(result==result_test) $display("Output correct!");
    endtask

    initial
    begin
        testCase(-6'd5, -6'd7, 1'b1); // -5 > -7
        testCase(-6'd10, 6'd5, 1'b0); // -10 < 5
        testCase(6'd10, 6'd2, 1'b1); // 10 > 2
        testCase(6'd15, 6'd25, 1'b0); // 15 < 25
        @(negedge clock) #1;
        $stop;
    end
endmodule

```

**Figure 12: Greater Than Module Testbench Code**

 


Figure 13: Greater Than Module Waveform Diagram

Figure 12 depicts an example of one of my testbenches, which is for the *greater than* module. Figure 13 depicts the waveform diagram of the *greater than* module. I have tested four cases with varying inputs and results. Figure 13 shows the correct results in that it wave goes high and low when it should. The other modules, such as *less than*, *equal*, and *zero*, are similar in design. As such, I have placed screenshots of them in Appendix B along with their respective waveform diagrams.

```

1 module fsm_testbench();
2
3     // DUT signals
4     logic clock = 1'b0;
5     logic [2:0]instruct;
6     logic [2:0]out_instruct;
7
8     // Connect device to check
9     fsm_lab7 dutlab7(.clock(clock), .instruct(instruct), .out_instruct(out_instruct));
10
11     // Generate clock
12     always #50 clock <= ~clock;
13
14     // Generate inputs
15
16     // Create task to loop through all possible combinations
17     task testCase(input logic [2:0]instruct_test, input logic [2:0]out_instruct_test);
18         @(negedge clock);
19         instruct <= instruct_test;
20         @(posedge clock);
21         check: assert(instruct_test == out_instruct_test) $display("Output correct!");
22     endtask
23
24     initial
25     begin
26         testCase(3'b000, 3'b000);
27         testCase(3'b001, 3'b001);
28         testCase(3'b100, 3'b100);
29         testCase(3'b101, 3'b101);
30         testCase(3'b110, 3'b110);
31         testCase(3'b111, 3'b111);
32         @(negedge clock) #1;
33         $stop;
34     end
35 endmodule

```

Figure 14: Operations FSM Testbench Code

 


**Figure 15: Operations FSM Waveform Diagram**

Figure 14 depicts the testbench code that I wrote for my operations FSM. Essentially, I needed to ensure that the instructions that get inputted into the FSM is the same as the output. I tested each of the six different operations and got the expected results from the waveform diagram as shown in Figure 15.

```
8      logic mode, rst;
9      logic nA_LED, nB_LED, nR_LED, over_LED, LED_full, LED_empty;
10     logic [6:0] DA7, DA6, DA5, DA4, DA3, DA2;
11
12     // Connect device to check
13     toplevel_lab7 dutlab7(.clock(clock), .instruct(instruct), .A(A), .B(B), .button(button), .mode(mode), .rst(rst), .nA_LED(nA_LED), .nB_LED(nB_LED),
14     .nR_LED(nR_LED), .over_LED(over_LED), .LED_full(LED_full), .LED_empty(LED_empty), .DA7(DA7), .DA6(DA6), .DA5(DA5), .DA4(DA4))
15
16     // Generate clock
17     always #50 clock <= ~clock;
18
19     // Generate inputs
20
21     // Create task to loop through all possible combinations
22     task Write(input logic [2:0]instruct_test, input logic [5:0]in_A, input logic [5:0]in_B, input logic mode_test, input logic rst_test);
23     @(negedge clock);
24     mode <= mode_test;
25     instruct <= instruct_test;
26     A <= in_A;
27     B <= in_B;
28     rst <= rst_test;
29     repeat(3)@(negedge clock);
30     button <= 'b1;
31     repeat(3)@(negedge clock);
32     button <= 'b0;
33     repeat(5)@(negedge clock);
34     //@(posedge clock);
35     //check: assert() $display("Output correct!");
36
37     endtask
```

**Figure 16: Top-Level Module Testbench Code**



**Figure 17: Top-Level Module Waveform Diagram**

The top-level testbench is the most important testbench of this lab because it tests the functionality of every component and module. Initially, I created a testbench in which I manually inputted the values I wanted to test. By doing so, I was able to manually check the values myself for accuracy. I tested up to eight different values. I then checked each values corresponding output to make sure the correct LEDs went high and the operation modules correctly calculated



```

else if (out_instruct == 3'b000 and rise == 1'b1)
begin
    nA_LED <= nA_LED_Add;
    nB_LED <= nB_LED_Add;
    nR_LED <= nR_LED_Add;
    over_LED <= over_LED_Add;
    DA7 <= display7;
    DA6 <= display6;
    DA5 <= display5;
    DA4 <= display4;
    DA3 <= display3;
    DA2 <= display2;
end

```

**Figure 19: Top-Level Design Error**

Figure 19 depicts what caused the delay problem in my design. For each condition state, I added the rising edge of the push-button. The problem with adding the rising edge in the top-level is that I already had added it into my Read-Write FSM. By including the rising edge in both modules, I had created a race condition in which some of the values got displayed on the 7-segment while others did not. After removing the rising edge button push in the top-level, my output displayed on the 7-segment displays right after I pressed the push-button.

### Analysis:

For my testing procedure, I created two different testbenches for my top-level design. I created a static testbench for directed testing and a randomized testbench to see the results of my overall design. The randomized testbench is good for scalability of testbench for a large project. However, in terms of debugging and analyzing if the design outputs correctly, a directed testbench works better. By having a directed testbench, I can easily target functions that I think are not operating correctly and fix them accordingly.

Unit	Setup Time (ns)	Hold Time (ns)	Maximum Clock Rate	Total Logic Elements	Total Register
Adder	-1.990	3.301	N/A	7	0
Subtractor	-2.992	3.404	N/A	13	0
Operations FSM	6.347	0.672	$2.25 \times 10^8$	14	5
Top-Level	-5.739	0.184	$2.26 \times 10^8$	510	198

**Figure 20: Timing Analyzer Data**



I have obtained the data on the adder and subtractor through the timing analyzer. From my analysis, the subtractor takes more time and uses more space overall. The subtractor has a higher setup time and hold time, which means it takes longer to before data gets inputted into my system and calculations start. Because the adder and subtractor do not have flip-flops, they do not have any clock rates to report. The subtractor takes up almost twice as much space, or logical elements, than the adder. The reason that the subtractor takes more space and time is because it performs a two's complement calculation on the input variable, B before doing any calculations. The adder simply adds the two input values.

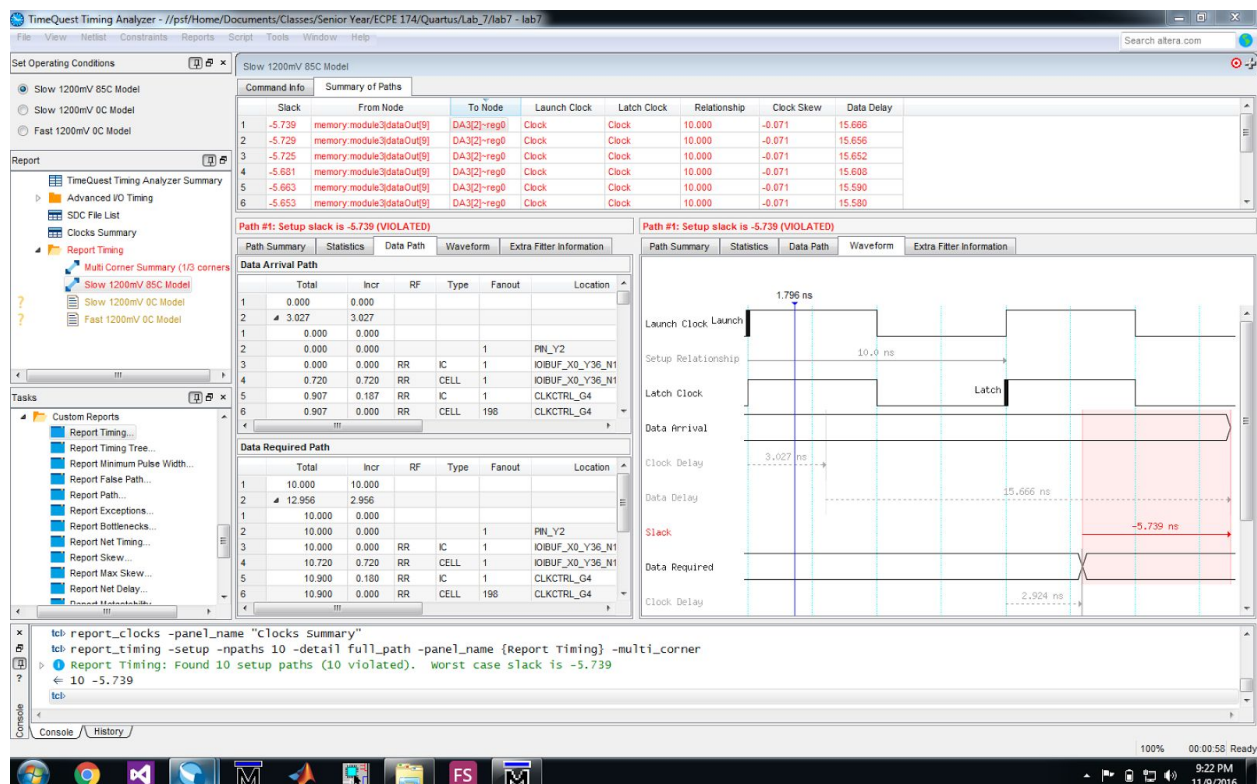


Figure 21: Timing Analyzer

Overall, my system design worked correctly and had been verified on the Cyclone Board. I used the timing analyzer to obtain data on the adder, subtractor, operations FSM, and top-level design. All the data can be found in Figure 20. The maximum clock frequency is taking the minimum pulse width and inverting it. So the equation is  $1/(\text{minimum pulse width})$ . My longest path is from my memory module (memory:module3|dataOut[9]) to my display (DA3[2]~reg0). The longest propagation delay for my top-level design is 15.739ns. The max slack is 5.739ns. I ran my timing analyzer for 10ns. Therefore, I added 10ns to 5.739ns for the longest path. The best way to reduce the propagation delay is to reduce the number of transitions throughout my design. It would involve making my code more efficient and using less flip-flops if they are not necessary.

## Appendix A: Additional Design

```
19 always_comb
20 begin
21     case(state)
22     IDLE:
23         if (mode==1'b0 && button==1'b1 && empty==1'b0)
24             nextstate = READ;
25         else if (mode==1'b1 && button==1'b1 && full==1'b0)
26             nextstate = WRITE;
27         else
28             nextstate = IDLE;
29     READ:
30         if (mode==1'b0 && button==1'b1 && empty==1'b0)
31             nextstate = READ;
32         else
33             nextstate = IDLE;
34     WRITE:
35         if (mode==1'b1 && button==1'b1 && full==1'b0)
36             nextstate = WRITE;
37         else
38             nextstate = IDLE;
39     default: nextstate = IDLE;
40 endcase
41 end
```

Figure A-1: Read-Write FSM Code Snippet

```
1 module synchronizer_lab7 (input logic clock,
2                           input logic button, rstsync,
3                           output logic rise);
4
5     logic in_ff1, in_ff2, in_ff3; // in_ff2 == in_sync1, in_ff3 == in_sync2
6
7     assign rise = (in_ff2 && !in_ff3);
8
9     always_ff @ (posedge clock or negedge rstsync)
10     begin
11         if (rstsync == 1'b0)
12         begin
13             in_ff1 <= 1'b0;
14             in_ff2 <= 1'b0;
15             in_ff3 <= 1'b0;
16         end
17         else
18         begin
19             in_ff1 <= button;
20             in_ff2 <= in_ff1;
21             in_ff3 <= in_ff2;
22         end
23     end
24 endmodule
```

Figure A-2: Synchronizer Code Snippet



```

1  module less (input logic [5:0]A,
2               input logic [5:0]B,
3               output logic [5:0]result,
4               output logic nA_LED, nB_LED);
5
6     logic [5:0]new_A;
7     logic [5:0]new_B;
8
9     always_comb
10    begin
11        if (A[5] == 1'b1)
12            new_A = ~A+1'b1;
13        else
14            new_A = A;
15    end
16
17    always_comb
18    begin
19        if (B[5] == 1'b1)
20            new_B = ~B+1'b1;
21        else
22            new_B = B;
23    end
24
25    always_comb
26    begin
27        if (A[5] == B[5] && A[5] == 1'b0)
28            begin
29                if (new_A < new_B)
30                    result = 6'd1;
31                else
32                    result = 6'd0;
33            end
34        else if (A[5] == B[5] && A[5] == 1'b1)
35            begin
36                if (new_A < new_B)

```

**Figure A-3: Less Than Module Code Snippet**

```

1  module adder ( input logic [5:0]A,
2                 input logic [5:0]B,
3                 output logic [5:0]out_val,
4                 output logic nA_LED, nB_LED, nR_LED,
5                 output logic over_LED);
6
7     assign out_val = A + B;
8

```

**Figure A-4: Adder Module Code Snippet**

```

1  module subtractor (input logic [5:0]A,
2                     input logic [5:0]B,
3                     output logic [5:0]out_val,
4                     output logic nA_LED, nB_LED, nR_LED,
5                     output logic over_LED);
6
7     logic [5:0]new_B;
8     assign new_B = (~B+1'b1);
9
10    assign out_val = A + (~B+1'b1);
11

```

**Figure A-5: Subtractor Module Code Snippet**

## Appendix B: ModelSim Testbenches and Waveform Diagrams

```
1 module less_testbench();
2
3     // DUT signals
4     logic clock = 1'b0;
5     logic [5:0]A;
6     logic [5:0]B;
7     logic result;
8
9     // Connect device to check
10    less dutlab7(.A(A), .B(B), .result(result));
11
12    // Generate clock
13    always #50 clock <= ~clock;
14
15    // Generate inputs
16
17    // Create task to loop through all possible combinations
18    task testCase(input logic [5:0]in_A, input logic [5:0]in_B, input logic result_test);
19        @(negedge clock);
20        A <= in_A;
21        B <= in_B;
22        @(posedge clock);
23        check: assert(result==result_test) $display("Output correct!");
24    endtask
25
26    initial
27    begin
28        testCase(-6'd5, -6'd7, 1'b0); // -5 > -7
29        testCase(-6'd10, 6'd5, 1'b1); // -10 < 5
30        testCase(6'd10, 6'd2, 1'b0); // 10 > 2
31        testCase(6'd15, 6'd25, 1'b1); // 15 < 25
32        @(negedge clock) #1;
33        $stop;
34    end
35
36 endmodule
```

Figure B-1: Less Than Module Testbench Code

 



Figure B-2: Less Than Module Waveform Diagram

```

1 module equal_testbench();
2
3     // DUT signals
4     logic clock = 1'b0;
5     logic [5:0]A;
6     logic [5:0]B;
7     logic result;
8
9     // Connect device to check
10    equal dutlab7(.A(A), .B(B), .result(result));
11
12    // Generate clock
13    always #50 clock <= ~clock;
14
15    // Generate inputs
16
17    // Create task to loop through all possible combinations
18    task testCase(input logic [5:0]in_A, input logic [5:0]in_B, input logic result_test);
19        @(negedge clock);
20        A <= in_A;
21        B <= in_B;
22        @(posedge clock);
23        check: assert(result==result_test) $display("Output correct!");
24
25    endtask
26
27    initial
28        begin
29            testCase(-6'd5, -6'd7, 1'b0); // -5 != -7
30            testCase(-6'd10, 6'd5, 1'b0); // -10 != 5
31            testCase(6'd18, 6'd18, 1'b1);
32            testCase(-6'd10, -6'd10, 1'b1);
33            testCase(6'd10, 6'd2, 1'b0); // 10 != 2
34            testCase(6'd15, 6'd25, 1'b0); // 15 != 25
35            @(negedge clock) #1;
36            $stop;
37        end

```

**Figure B-3: Equal Module Testbench Code**

 


**Figure B-4: Equal Module Waveform Diagram**

```

1 module zero_testbench();
2
3     // DUT signals
4     logic clock = 1'b0;
5     logic [5:0]A;
6     logic result;
7
8     // Connect device to check
9     zero dutlab7(.A(A), .result(result));
10
11    // Generate clock
12    always #50 clock <= ~clock;
13
14    // Generate inputs
15
16    // Create task to loop through all possible combinations
17    task testCase(input logic [5:0]in_A, input logic result_test);
18        @(negedge clock);
19        A <= in_A;
20        @(posedge clock);
21        check: assert(result==result_test) $display("Output correct!");
22
23    endtask
24
25    initial
26    begin
27        testCase(-6'd5, 1'b0); // false
28        testCase(6'd0, 1'b1); // true
29        testCase(-6'd10, 1'b1); // false
30        testCase(6'd0, 1'b0); // true
31        @(negedge clock) #1;
32        $stop;
33    end
34 endmodule
35

```

**Figure B-5: Zero Module Testbench Code**

 

**Figure B-6: Zero Module Waveform Diagram**

```

43         endcase*/
44         instruct <= $urandom_range(7,0);
45         in_A = $urandom_range(63,0);
46         in_A = in_A - 6'd32;
47         in_B = $urandom_range(63,0);
48         in_B = in_B - 6'd32;
49
50         //rst <= $urandom_range(1,0);
51         rst <= 1'b1;
52         mode <= $urandom_range(1,0);
53
54         //instruct <= instructVal;
55         //mode <= mode_test;
56         A <= in_A;
57         B <= in_B;
58         //rst <= rst_test;|
59         repeat(3)@(negedge clock);
60         button <= 1'b1;
61         repeat($urandom_range(5,1))@(negedge clock);
62         button <= 1'b0;
63         repeat($urandom_range(5,1))@(negedge clock);
64     endtask
65
66     initial
67     begin
68
69         rand_loop=$urandom_range(300, 10);
70         for(int i=0; i<rand_loop; i++)
71             begin
72                 TestEverything();
73             end
74         repeat(10)@(negedge clock) #1;
75         $stop;
76
77     end
78 endmodule
79

```

**Figure B-7: Top-Level Module with Randomization Testbench Code**